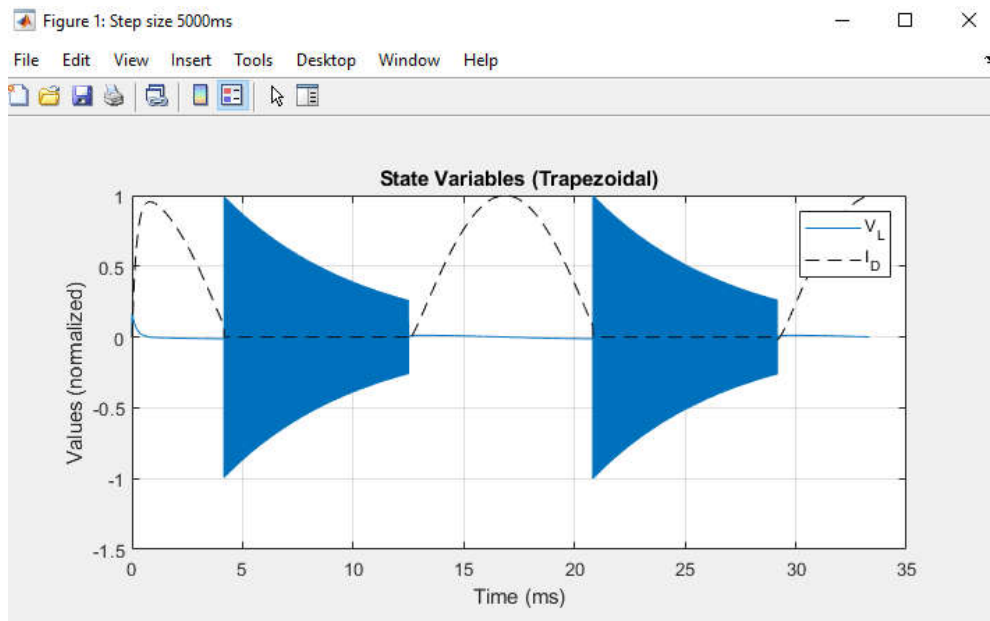


CRES Assignment 6

Submitted by: Hutomo Saleh

The simulation using trapezoidal method returns a heavily distorted result. The oscillation during the blocking of the diode is due to the history variable of the trapezoidal method.




The derivation of the backward-euler method is as follows:


$$\begin{aligned}
 \frac{V(k) - V(k-1)}{\tau} &= \eta \cdot i(k) \\
 i(k) &= \left(\frac{1}{\eta \tau} \right) (V(k) - V(k-1)) \\
 &\quad \downarrow G \\
 &= \frac{1}{\eta \tau} V(k) - \frac{1}{\eta \tau} V(k-1) \\
 &\quad \downarrow \\
 &= G \cdot V(k) - \eta \\
 \Rightarrow G &= \frac{1}{\eta \tau} \quad \text{and} \quad \eta = G \cdot V(k-1) \\
 \text{For } L &\Rightarrow G_L = \frac{\tau}{L} \\
 C &\Rightarrow G_C = \frac{C}{\tau}
 \end{aligned}$$

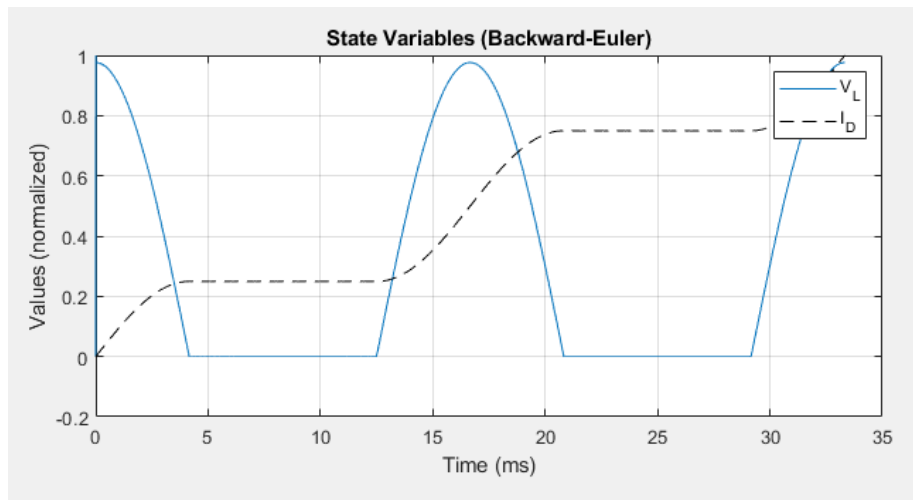[1.0]

The backward-Euler method shows that the voltage across the inductor does not oscillate, unlike the result using the trapezoidal method.



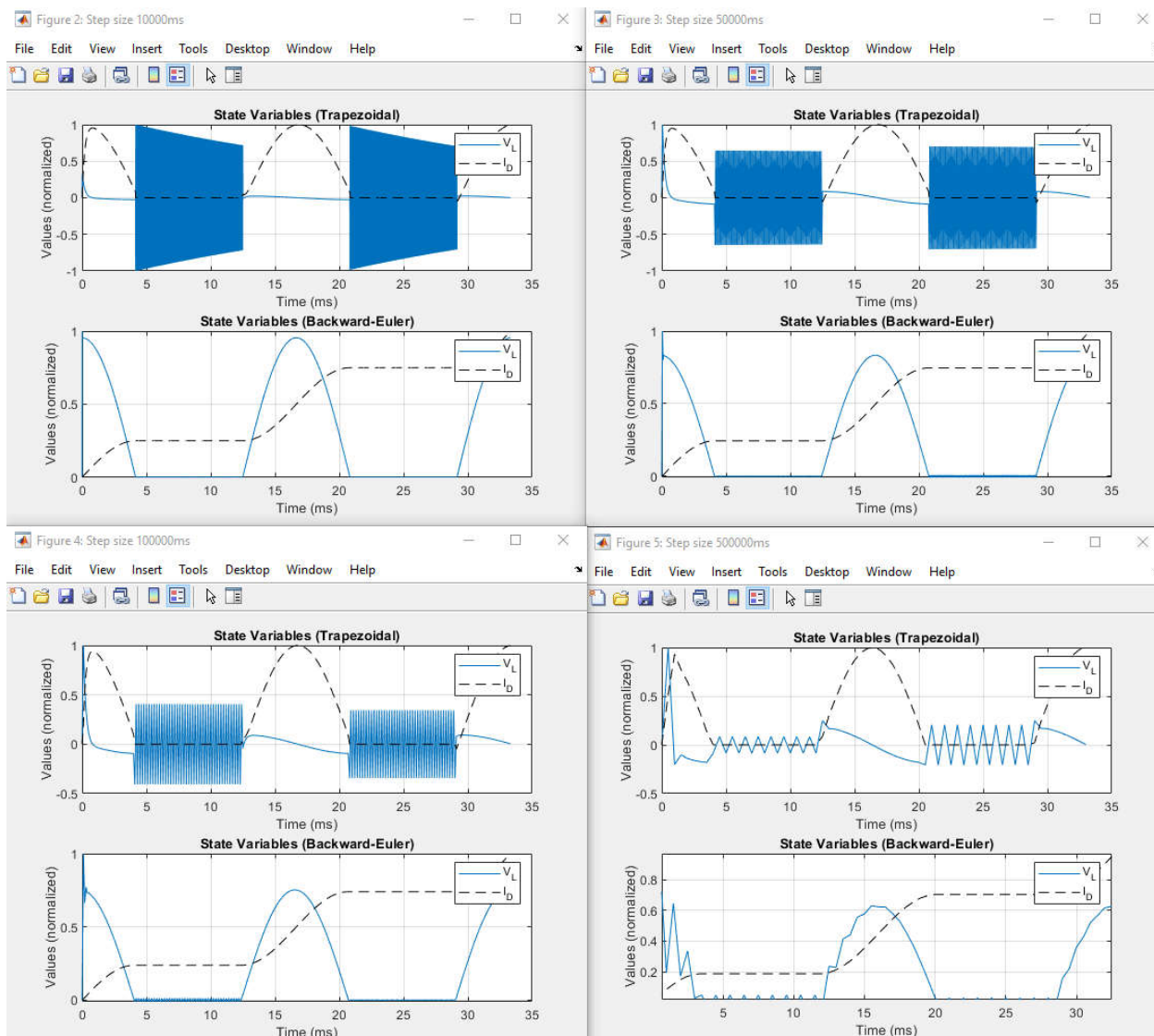Generally, the accuracy of the approximation will increase with smaller time step sizes. This is why with successively larger time step size, the oscillation as well as distortions will be seen more clearly.



For C), the chosen step sizes are $5\mu\text{s}$, $10\mu\text{s}$, $50\mu\text{s}$, 0.1ms and 0.5ms . It is shown in the figures that with increasing step size, the oscillation or distortion in the trapezoidal method becomes more spaced. At the largest step size of 0.5ms it is even shown that using backward euler-method results in oscillation, this is probably due to the step size nearing the

MATLAB Code

The whole code will be shown at the end of this document. This part will only show the important changes applied to the existing code from assignment 5.

The values of the diode admittance is separated into two parts for ON and OFF.

```
12
13 -   D.val.off = 1e-6;
14 -   D.val.on = 1e3;
15 -   D.node1 = 2;
16 -   D.node2 = 3;
17 -   D.n = 1;
18
```

The value of the diode will alternate depending on the value of voltage source. As shown below:

```
82 -   for i = 1:V.n
83 -       V.val(i) = V.mag(i) * cos(2 * pi * f * k * t.step + V.phase(i));
84 -       %% Change value of Diode depending on Voltage
85 -       if V.val(i) < 0
86 -           % disp("Voltage is minus")
87 -           D.Y = D.val.off(1:D.n);
88 -       else
89 -           % disp("Voltage is positive")
90 -           D.Y = D.val.on(1:D.n);
91 -       end
92 -       node.e(i) = V.node1(i); % Get excitation nodes
93 -   end
```

When applying the backward-Euler method, the admittance calculation of inductor must be changed according to the derivation showed in [1.0].

```

77 - L.Y = t.step / (loop * L.val(1:L.n)); % Derived (4.23) but w/ inductor
78 - C.Y = loop * C.val(1:C.n) / t.step; % From (4.26)

104 %% Update current values (according to 4.22-4.28)
105 I.mag = zeros(node.n, 1);
106 for i = 1:I.n
107     I.mag(I.node1(i)) = I.mag(i) * ...
108         cos(2 * pi * f * k * t.step + I.phase(i));
109     I.mag(I.node2(i)) = -I.mag(I.node1(i));
110 end
111 for i = 1:2:L.n % Increments of two due to V and I
112     eta = L.Y * trans.val(k-1, i) + trans.val(k-1, i+1);
113     if loop == 1 % backward-euler
114         eta = L.Y * trans.val(k-1, i);
115     end
116     I.mag(L.node1(i)) = I.mag(L.node1(i)) - eta;
117     I.mag(L.node2(i)) = I.mag(L.node2(i)) + eta;
118 end
119 for i = 1:2:C.n
120     C_index = 2 * L.n + i;
121     eta = C.Y * trans.val(k-1, C_index) + trans.val(k-1, C_index+1);
122     if loop == 1 % backward-euler
123         eta = C.Y * trans.val(k-1, C_index);
124     end
125     I.mag(C.node1(i)) = I.mag(C.node1(i)) + eta;
126     I.mag(C.node2(i)) = I.mag(C.node2(i)) - eta;
127 end

```

Full MATLAB Code

```

1 - clc;
2 - close all;
3 - clear all;
4
5 %% Variable Initialization
6 % {
7     n: Amount
8     val: Value
9     mag: Magnitude
10    node1 / node2: 1st (start) / 2nd (end) Node
11 % }
12
13 D.val.off = 1e-6;
14 D.val.on = 1e3;
15 D.node1 = 2;
16 D.node2 = 3;
17 D.n = 1;
18
19 G.val = 0.2;
20 G.node1 = 1;
21 G.node2 = 4;
22 G.n = 1;
23
24 L.val = 1e-3;
25 L.node1 = 2;
26 L.node2 = 1;
27 L.n = 1;
28
29 C.val = [];
30 C.node1 = [];
31 C.node2 = [];
32 C.n = 0;
33
34 V.mag = 230e3;
35 V.phase = 0;
36 V.node1 = 3;
37 V.node2 = 4;
38 V.n = 1;
39
40 I.mag = [];
41 I.phase = [];
42 I.node1 = [];
43 I.node2 = [];
44 I.n = 0;
45
46 normalized = true;
47 node.n = D.n + G.n + L.n + C.n + 1;
48 f = 60;
49
50 %% Calculation - A & B
51 % Diode Model Simulation using Trapezoidal & Backward-Euler Method
52 step_sizes = [5e-6 1e-5 5e-5 1e-4 5e-4];
53 % step_sizes = [5e-6];
54
55

```

```

55
56 - for step = 1:length(step_sizes)
57     %% Initialization
58     t.step = step_sizes(step); % time step
59     t.span = 0:t.step:(2/60);
60     t.len = length(t.span);
61
62     trans.n = (L.n + C.n) * 2; % For V and I of each trans. elements
63     trans.val = zeros(t.len, trans.n); % Value of transient elements (V, I)
64     V.nodeval = zeros(t.len, node.n); % Voltage of each nodes
65     plot_title = ["(Backward-Euler)" "(Trapezoidal)"];
66
67 - for loop = 1:2
68
69     %|
70     Loop 1: Backward-Euler
71     Loop 2: Trapezoidal Method
72     %|
73
74     % Setup admittance values
75     G.Y = G.val(1:G.n); % No transient effect
76     D.Y = D.val.on(1:D.n); % No transient effect
77     L.Y = t.step / (loop * L.val(1:L.n)); % Derived (4.23) but w/ inductor
78     C.Y = loop * C.val(1:C.n) / t.step; % From (4.26)
79
80 - for k = 2:t.len % 1st index already defined
81     V.val = zeros(V.n+1, 1);
82     for i = 1:V.n
83         V.val(i) = V.mag(i) * cos(2 * pi * f * k * t.step + V.phase(i));
84         %% Change value of Diode depending on Voltage
85         if V.val(i) < 0
86             % disp("Voltage is minus")
87             D.Y = D.val.off(1:D.n);
88         else
89             % disp("Voltage is positive")
90             D.Y = D.val.on(1:D.n);
91         end
92         node.e(i) = V.node1(i); % Get excitation nodes
93     end
94     node.e(V.n + 1) = node.n; % Insert ground node
95     node.d = zeros(node.n - length(node.e), 1); % Make dependent nodes
96     l = 1;
97     for i = 1:node.n % Loop through nodes
98         if isempty(find(node.e == i, 1)) % If dependent nodes, insert
99             node.d(l) = i;
100             l = l + 1;
101         end
102     end
103
104     %% Update current values (according to 4.22-4.28)
105     I.mag = zeros(node.n, 1);
106     for i = 1:I.n
107         I.mag(I.node1(i)) = I.mag(i) * ...
108             cos(2 * pi * f * k * t.step + I.phase(i));
109         I.mag(I.node2(i)) = -I.mag(I.node1(i));
110     end
111     for i = 1:2:L.n % Increments of two due to V and I
112         eta = L.Y * trans.val(k-1, i) + trans.val(k-1, i+1);
113         if loop == 1 % backward-euler
114             eta = L.Y * trans.val(k-1, i);
115         end
116         I.mag(L.node1(i)) = I.mag(L.node1(i)) - eta;
117         I.mag(L.node2(i)) = I.mag(L.node2(i)) + eta;
118     end
119     for i = 1:2:C.n
120         C_index = 2 * L.n + i;

```



```

119-     for i = 1:2:C.n
120-         C_index = 2 * L.n + i;
121-         eta = C.Y * trans.val(k-1, C_index) + trans.val(k-1, C_index+1);
122-         if loop == 1 % backward-euler
123-             eta = C.Y * trans.val(k-1, C_index);
124-         end
125-         I_mag(C.node1(i)) = I_mag(C.node1(i)) + eta;
126-         I_mag(C.node2(i)) = I_mag(C.node2(i)) - eta;
127-     end
128-
129-     % Setup admittance matrix
130-     Ymat = zeros(node.n, node.n);
131-     Ymat = updateYMatrix(Ymat, G);
132-     Ymat = updateYMatrix(Ymat, D);
133-     Ymat = updateYMatrix(Ymat, L);
134-     Ymat = updateYMatrix(Ymat, C);
135-
136-     Y = Ymat(node.d, node.d);
137-     I_d = I_mag(node.d);
138-     Yde = Ymat(node.d, node.e);
139-     I_mag = I_d - Yde * V.val;
140-
141-     V.d = Y \ I_mag; % Solve dependent node voltage
142-
143-     %% Update node voltages
144-     n = length(node.d); % Insert dependent values
145-     for i=1:n
146-         V.nodeval(k, node.d(i)) = V.d(i);
147-     end
148-     V.nodeval(k, 3) = V.val(1);
149-     V.nodeval(k, 4) = 0.0;
150-
151-     %% Calculate transient values
152-     for i = 1:2:L.n
153-         eta = L.Y * trans.val(k-1, i) + trans.val(k-1, i+1); % (4.27)
154-         V_L = V.nodeval(k, L.node1(i)) - V.nodeval(k, L.node2(i));
155-         I_L = L.Y * V_L + eta;
156-
157-         trans.val(k, i) = V_L;
158-         trans.val(k, i+1) = I_L;
159-     end
160-     for i = 1:2:C.n
161-         C_index = 2 * L.n + i;
162-         eta = C.Y * trans.val(k-1, C_index) + trans.val(k-1, C_index+1);
163-         V_C = V.nodeval(k, C.node1(i)) - V.nodeval(k, C.node2(i));
164-         I_C = C.Y * V_C - eta;
165-
166-         trans.val(k, C_index) = V_C;
167-         trans.val(k, C_index+1) = I_C;
168-     end
169- end
170-
171- %% Normalize values
172- y_label = 'Voltage [V] and Current [A]';
173- if (normalized == true)
174-     y_label = 'Values (normalized)';
175-     for i = 1:node.n-1
176-         V.nodeval(:, i) = V.nodeval(:, i) / max(V.nodeval(:, i));
177-     end
178-     for i = 1:trans.n
179-         trans.val(:, i) = trans.val(:, i) / max(trans.val(:, i));
180-     end
181- end
182-

```

```

182
183     if loop == 2
184         y_plot_TV = trans.val(:, 1);
185         y_plot_TI = trans.val(:, 2);
186     else
187         y_plot_BV = trans.val(:, 1);
188         y_plot_BI = trans.val(:, 2);
189     end
190 end
191
192 %% Plot
193 fig_title = "Step size " + sprintf("%.0f", (t.step*1e9)) + 'ms';
194 figure("name", fig_title);
195 subplot(211)
196 x_plot = t.span*1e3;
197 plot(x_plot, y_plot_TV, x_plot, y_plot_TI, 'k--');
198 grid on;
199 legend('V_L', 'I_D');
200 title('State Variables (Trapezoidal)');
201 ylabel(y_label);
202 xlabel('Time (ms)');
203
204 subplot(212)
205 plot(x_plot, y_plot_BV, x_plot, y_plot_BI, 'k--');
206 grid on;
207 legend('V_L', 'I_D');
208 title('State Variables (Backward-Euler)');
209 ylabel(y_label);
210 xlabel('Time (ms)');
211 end
212
213 %% Functions
214 function Y_out = updateYMatrix(Y_in, Y)
215     for i = 1:Y.n
216         % Diagonal elements(same index): positive. Else negative.
217         Y_in(Y.node1(i), Y.node1(i)) = Y_in(Y.node1(i), Y.node1(i)) + Y.Y(i);
218         Y_in(Y.node2(i), Y.node2(i)) = Y_in(Y.node2(i), Y.node2(i)) + Y.Y(i);
219         Y_in(Y.node1(i), Y.node2(i)) = Y_in(Y.node1(i), Y.node2(i)) - Y.Y(i);
220         Y_in(Y.node2(i), Y.node1(i)) = Y_in(Y.node2(i), Y.node1(i)) - Y.Y(i);
221     end
222     Y_out = Y_in;
223 end

```