

CRES Assignment 5

Submitted by: Hutomo Saleh

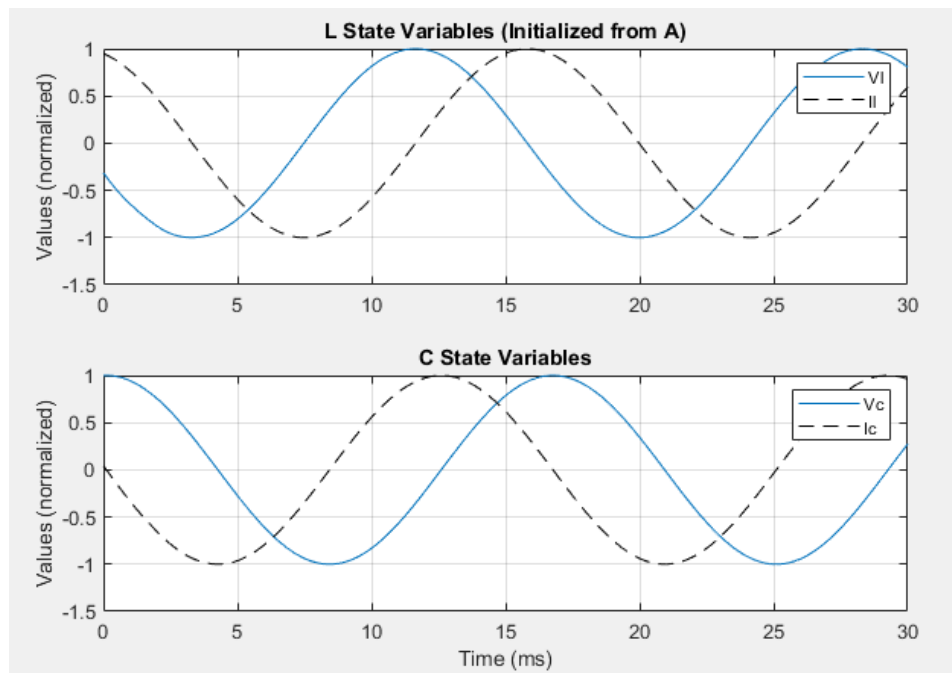


Figure 1: Plot using state variables from A)

C) Discussion:

As shown in Figure 1. Due to the steady state initialized from A), there is no transient seen at the beginning of the curve. In comparison with Figure 2, C) starts with $V_C = 0$ and $I_L = 0$, which causes a transient in the first few ms, due to the nature of not being able to change instantaneously.

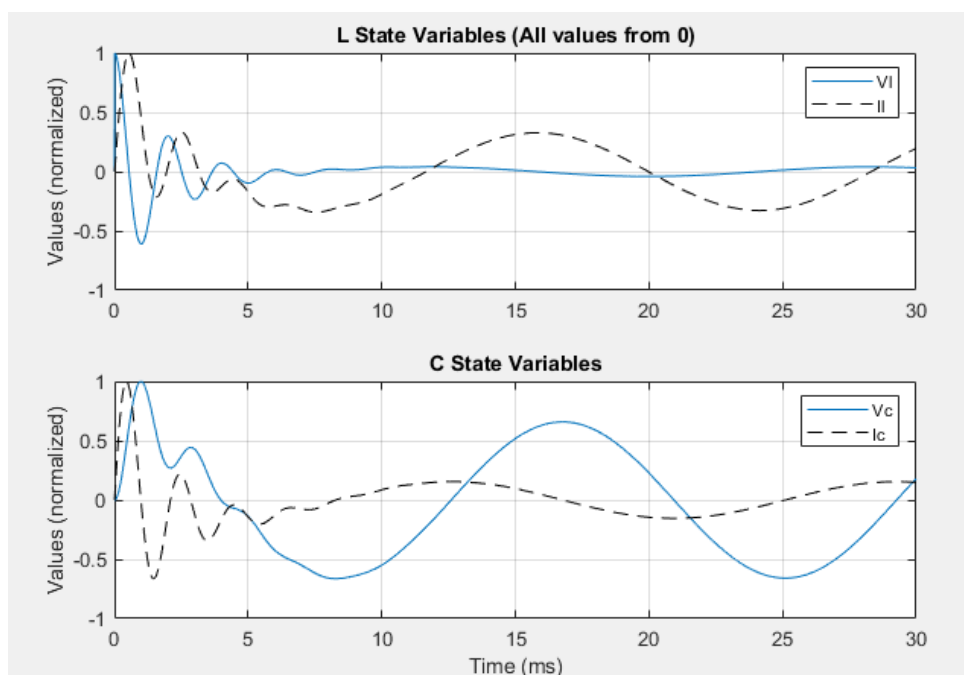


Figure 2: Plot using state variables of 0

Matlab Code

```

1 - clc;
2 - close all;
3 - clear all;
4
5 %% Discussion on B) and C)
6 % Due to the steady state initialized from A), there is no transient
7 % seen at the beginning of the curve. In comparison, C) starts with
8 %  $V_c = 0$  and  $i_L = 0$ , which causes a transient in the first few ms,
9 % due to the nature of not being able to change instantaneously.
10
11 %% Variable Initialization
12 % {
13     n: Amount
14     val: Value
15     mag: Magnitude
16     node1 / node2: 1st (start) / 2nd (end) Node
17 % }
18
19 normalized = true;
20 node.n = 4;
21 f = 60;
22
23 G.val = [1 0.01];
24 G.node1 = [1 2];
25 G.node2 = [3 4];
26 G.n = 2;
27
28 L.val = 10e-3;
29 L.node1 = 1;
30 L.node2 = 2;
31 L.n = 1;
32
33 C.val = 10e-6;
34 C.node1 = 2;
35 C.node2 = 4;
36 C.n = 1;
37
38 V.mag = 230e3;
39 V.phase = 0;
40 V.node1 = 3;
41 V.node2 = 4;
42 V.n = 1;
43
44 I.mag = [];
45 I.phase = [];
46 I.node1 = [];
47 I.node2 = [];
48 I.n = 0;
49
50 %% Calculation - A
51
52 % Setup admittance matrix
53 Yorg = zeros(node.n, node.n); % Preallocate matrix size
54 G.Y = G.val(1:G.n);
55 Yorg = updateYMatrix(Yorg, G);
56 L.Y = 1 / (1j * 2 * pi * f * L.val(1:L.n));
57 Yorg = updateYMatrix(Yorg, L);
58 C.Y = 1j * 2 * pi * f * C.val(1:C.n);
59 Yorg = updateYMatrix(Yorg, C);
60
61 V.val = zeros(V.n + 1, 1); % Preallocate Voltage matrix
62 node.e = zeros(V.n + 1, 1); % Make excitation nodes

```

```

63
64     % Voltage Source
65 -   for i = 1:V.n
66 -       V.val(i) = V.mag(i) * exp(1j * V.phase(i)); % Get voltage value
67 -       node.e(i) = V.node1(i); % Get excitation nodes
68 -   end
69 -   node.e(V.n + 1) = node.n; % Insert ground node
70
71 -   node.d = zeros(node.n - length(node.e), 1); % Make dependent nodes
72 -   k = 1;
73 -   for i = 1:node.n % Loop through nodes
74 -       if isempty(find(node.e == i, 1)) % If dependent nodes, insert
75 -           node.d(k) = i;
76 -           k = k + 1;
77 -       end
78 -   end
79
80     % Current source
81 -   I.mag = zeros(node.n, 1);
82 -   for i = 1:I.n
83 -       I.mag(I.node1(i)) = I.mag(i) * exp(1j * I.phase(i));
84 -       I.mag(I.node2(i)) = -I.mag(I.node1(i));
85 -   end
86
87     % Make dependent variables (4.12)
88 -   Y = Yorg(node.d, node.d);
89 -   Yde = Yorg(node.d, node.e);
90 -   I.d = I.mag(node.d);
91 -   I.mag = I.d - Yde * V.val;
92
93     % Solve dependent voltage (4.16)
94 -   V.d = Y \ I.mag; % Matrix left division from I.mag * V.d = Ydep
95
96     % Calculate branch currents
97 -   V1 = V.d(1);
98 -   V2 = V.d(2);
99 -   I.L = (V1 - V2) / (1j * 2 * pi * f * L.val);
100 -   I.C = V2 * 1j * 2 * pi * f * C.val;
101
102     % Results
103 -   V1 = real(V1);
104 -   V2 = real(V2);
105 -   I.L = real(I.L);
106 -   I.C = real(I.C);
107
108 -   disp("V1: " + V1*1e-3 + " kV");
109 -   disp("V2: " + V2*1e-3 + " kV");
110 -   disp("iL: " + I.L + " A");
111 -   disp("iC: " + I.C + " A");
112
113 %% Calculation - B
114 % Electromagnetic Transients Simulation
115
116 -   for loop = 1:2 % For B) & C)
117       %% Initialization
118       t.step = 1e-5; % time step
119       t.span = 0:t.step:0.03;
120       t.len = length(t.span);
121
122       trans.n = (L.n + C.n) * 2; % For V and I of each trans. elements
123       trans.val = zeros(t.len, trans.n); % Value of transient elements (V, I)
124       V.nodeval = zeros(t.len, node.n); % Voltage of each nodes

```

```

125
126 if (loop==1)
127     % Initialize with values from A]
128     window_title = "Plot for B)";
129     plot_title = " (Initialized from A)";
130     trans.val(1, :) = [V1-V2 I.L V2 I.C]; % V1, I1, Vc, Ic
131     V.nodeval(1, :) = [V1 V2 V.mag 0];
132 elseif (loop==2)
133     % Initialization for C)
134     window_title = "Plot for C)";
135     plot_title = " (All values from 0)";
136 end
137
138 % Setup admittance matrix (Using trapezoidal method)
139 Yorg = zeros(node.n, node.n);
140 G.Y = G.val(1:G.n); % No transient effect
141 Yorg = updateYMatrix(Yorg, G);
142 L.Y = t.step / (2 * L.val(1:L.n)); % Derived (4.23) but w/ inductor
143 Yorg = updateYMatrix(Yorg, L);
144 C.Y = 2 * C.val(1:C.n) / t.step; % From (4.26)
145 Yorg = updateYMatrix(Yorg, C);
146
147
148 for k = 2:t.len % 1st index already defined
149     %% Update voltage values
150     V.val = zeros(V.n+1, 1);
151
152     for i = 1:V.n
153         V.val(i) = V.mag(i) * cos(2 * pi * f * k * t.step + V.phase(i));
154     end
155
156     %% Update current values (according to 4.22-4.28)
157     I.mag = zeros(node.n, 1);
158     for i = 1:I.n
159         I.mag(I.node1(i)) = I.mag(i) * ...
160             cos(2 * pi * f * k * t.step + I.phase(i));
161         I.mag(I.node2(i)) = -I.mag(I.node1(i));
162     end
163     for i = 1:2:L.n % Increments of two due to V and I
164         eta = L.Y * trans.val(k-1, i) + trans.val(k-1, i+1);
165         I.mag(L.node1(i)) = I.mag(L.node1(i)) - eta;
166         I.mag(L.node2(i)) = I.mag(L.node2(i)) + eta;
167     end
168     for i = 1:2:C.n
169         C_index = 2 * L.n + i;
170         eta = C.Y * trans.val(k-1, C_index) + trans.val(k-1, C_index+1);
171         I.mag(C.node1(i)) = I.mag(C.node1(i)) + eta;
172         I.mag(C.node2(i)) = I.mag(C.node2(i)) - eta;
173     end
174
175     %% Dependant nodes taken from A)
176     Y = Yorg(node.d, node.d);
177     I.d = I.mag(node.d);
178     Yde = Yorg(node.d, node.e);
179     I.mag = I.d - Yde * V.val;
180
181     V.d = Y \ I.mag; % Solve dependent node voltage
182
183     %% Update node voltages
184     n = length(node.d); % Insert dependent values
185     for i=1:n
186         V.nodeval(k, node.d(i)) = V.d(i);

```

```

187 -         end
188 -         V.nodeval(k, 3) = V.val(1);
189 -         V.nodeval(k, 4) = 0.0;
190 -
191 -         %% Calculate transient values
192 -         for i = 1:2:L.n
193 -             eta = L.Y * trans.val(k-1, i) + trans.val(k-1, i+1); % (4.27)
194 -             V_L = V.nodeval(k, L.node1(i)) - V.nodeval(k, L.node2(i));
195 -             I_L = L.Y * V_L + eta;
196 -
197 -             trans.val(k, i) = V_L;
198 -             trans.val(k, i+1) = I_L;
199 -         end
200 -         for i = 1:2:C.n
201 -             C_index = 2 * L.n + i;
202 -             eta = C.Y * trans.val(k-1, C_index) + trans.val(k-1, C_index+1);
203 -             V_C = V.nodeval(k, C.node1(i)) - V.nodeval(k, C.node2(i));
204 -             I_C = C.Y * V_C - eta;
205 -
206 -             trans.val(k, C_index) = V_C;
207 -             trans.val(k, C_index+1) = I_C;
208 -         end
209 -     end
210 -
211 -     %% Normalize values
212 -     y_label = 'Voltage [V] and Current [A]';
213 -     if (normalized == true)
214 -         y_label = 'Values (normalized)';
215 -         for i = 1:node.n-1
216 -             V.nodeval(:, i) = V.nodeval(:, i) / max(V.nodeval(:, i));
217 -         end
218 -         for i = 1:trans.n
219 -             trans.val(:, i) = trans.val(:, i) / max(trans.val(:, i));
220 -         end
221 -     end
222 -
223 -     %% Plot
224 -     figure('name', window_title);
225 -     subplot(211);
226 -     x_plot = t.span*1e3;
227 -     plot(x_plot, trans.val(:, 1), x_plot, trans.val(:, 2), 'k--');
228 -     grid on;
229 -     legend('Vl', 'Il');
230 -     title('L State Variables' + plot_title);
231 -     ylabel(y_label);
232 -
233 -     subplot(212);
234 -     plot(x_plot, trans.val(:, 3), x_plot, trans.val(:, 4), 'k--');
235 -     grid on;
236 -     legend('Vc', 'Ic');
237 -     title('C State Variables');
238 -     xlabel('Time (ms)');
239 -     ylabel(y_label);
240 -
241 - end
242 -
243 - %% Functions
244 - function Y_out = updateYMatrix(Y_in, Y)
245 -     for i = 1:Y.n
246 -         % Diagonal elements(same index): positive. Else negative.
247 -         Y_in(Y.node1(i), Y.node1(i)) = Y_in(Y.node1(i), Y.node1(i)) + Y.Y(i);
248 -         Y_in(Y.node2(i), Y.node2(i)) = Y_in(Y.node2(i), Y.node2(i)) + Y.Y(i);
249 -         Y_in(Y.node1(i), Y.node2(i)) = Y_in(Y.node1(i), Y.node2(i)) - Y.Y(i);
250 -         Y_in(Y.node2(i), Y.node1(i)) = Y_in(Y.node2(i), Y.node1(i)) - Y.Y(i);
251 -     end
252 -     Y_out = Y_in;
253 - end

```