

Electric Networks: Computer Aided Analysis and Simulation

Prof. Kai Strunz, Faculty of Electrical Engineering and Computer Science, TU Berlin

Problem Sheet 7

January 2021

Given is the following pattern of an admittance matrix:

$$\mathbf{Y} = \begin{pmatrix} \times & 0 & \times & \times & \times \\ 0 & \times & \times & \times & \times \\ \times & \times & \times & 0 & 0 \\ \times & \times & 0 & \times & 0 \\ \times & \times & 0 & 0 & \times \end{pmatrix}$$

- Draw topological graph.
- Determine the factorized matrix \mathbf{Q} and mark the fill-in elements.
- Determine the factorization path graph for all nodes.
- Assume that between nodes 1 and 4 a diode is connected. Which rows and columns have to be refactorized when the status changes?
- Renumber the nodes of the topological graph with the aim to reduce the number of fill-in elements.
- Determine new \mathbf{Y} and \mathbf{Q} .
- Determine the new factorization path graph for all nodes.
- When the diode changes status now, which rows and columns of the new \mathbf{Q} have to be updated?