

Electric Networks: Computer Aided Analysis and Simulation

Prof. Kai Strunz, Faculty of Electrical Engineering and Computer Science, TU Berlin

Problem Sheet 3

November 2020

Consider the circuit in figure 1. The resistance is $R = 1\ \Omega$, the capacitance is $C = 10^{-3}\ F$, the initial condition of the capacitive voltage at $t = 0\ s$ is $v_C(0) = 10\ V$.

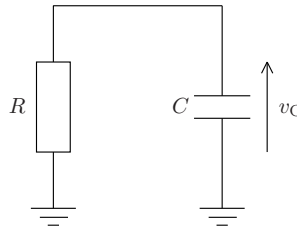



Figure 1

- 1 points** Derive an analytic expression for $v_C(t)$. Draw the waveform in the interval from $t = 0\ ms$ to $t = 10\ ms$ in a diagram. The use of a computational tools such as MATLAB is recommended.
- 4 points** Using the backward-Euler method, derive a difference equation to calculate $v_C(k)$. Select an appropriate time step size. Draw the graph of $v_C(t)$ over time t in the interval from $t = 0\ ms$ to $t = 10\ ms$ in the diagram of a). Discuss the selection of the time step size. 
- 4 points** Perform the same tasks as described under b), but use the trapezoidal and forward-Euler methods.
- 8 points** Draw all curves of a), b) and c) in the same diagram and zoom in, i. e. consider for example the region $0 \leq v_C \leq 10\ V$ and $0.5\ ms \leq t \leq 1\ ms$. Consider the accuracy of the results. Discuss how these experimental results relate to the analytical accuracy considerations of backward-Euler, forward-Euler and trapezoidal methods studied in problem sheet 1 and chapter 2 of the lecture notes.
- 2 points** Determine the value of the time step size above which the forward-Euler method becomes unstable. $\tau > |1 / \lambda|$
- 2 points** Determine the value of the time step size above which numerical oscillations are observed when using the trapezoidal method. $\tau > |2 / \lambda|$
- 4 points** Select the following time step size: $\tau = 2RC$. Draw the curves obtained for the backward-Euler, trapezoidal and forward-Euler methods over time t in the interval from $t = 0\ ms$ to $t = 20\ ms$. Discuss the results.
- 4 points** Select the following time step size: $\tau = 4RC$. Draw the curves obtained for the backward-Euler, trapezoidal and forward-Euler methods over time t in the interval from $t = 0\ ms$ to $t = 20\ ms$. Discuss the results.